

$$\frac{V_o}{V_i} = \frac{\frac{RCS + 1}{R_1CS} - 1}{\frac{RCS + 1}{2R_1CS} + 1}$$